

# **OPA564 Biasing Considerations During Enabled and Disabled States**

Ed Mullins

High-Performance Analog

## **ABSTRACT**

The [OPA564](#) is a high-voltage, high-current, wide-bandwidth operational amplifier suitable for many applications. Among the many features available on the OPA564 is a disabled mode that is designed to be used for power savings in time multiplexed systems such as powerline communications. When using an op amp that can be placed into either the enabled state or disabled state (shutdown), it is critical to define the biasing conditions in such a manner that any disturbances are minimized when making the transition between the two states. Additionally, it is critical to keep all of the device terminals within safe operating limits under all conditions. Failure to follow the guidelines discussed here could result in poor performance and potential damage to the OPA564.

## **Contents**

1	Introduction .....	1
2	Problem Description .....	2
3	Solutions .....	3
4	Conclusion .....	6

## **List of Figures**


1	Unity-Gain Powerline Communications Line Driver with DC-Coupled Load .....	2
2	Output Results for Improperly Configured Circuit.....	2
3	Unity-Gain Powerline Communications Line Driver with AC-Coupled Load .....	3
4	AC-Coupled, Inverting Gain Powerline Communications Line Driver with AC-Coupled Load .....	3
5	Output Results for Properly Configured Circuit (AC Load Only).....	4
6	AC-Coupled, Inverting Gain Powerline Communications Line Driver with AC-Coupled Load and Voltage Divider .....	4
7	Output Results for Properly Configured Circuit with Voltage Divider.....	5
8	Dual Supply, DC-Connected Load Unity-Gain Follower .....	5

## **1 Introduction**

Biasing an op amp during normal operation (that is, the device is in enabled mode) is generally straightforward: the biasing is defined by the desired transfer function that is required for the signal processing task at hand. Simple examples of such transfer functions might be a noninverting gain configuration, an inverting gain configuration, or a variety of other well-known op amp configurations. During shutdown, however, the function of the amplifier is to provide no relationship between the input and output, as well as to conserve as much power as possible. A correct design is required to prevent disturbances to the signal as it transitions between the enabled and disabled states, as well as ensure that the device is placed into a condition that does not cause damage to the amplifier during extended periods in the disabled state.


## 2 Problem Description

When an op amp transitions between an enabled and disabled state and back again, undesirable performance anomalies can be clearly observed if the design has not taken these transitions into account. As an example, consider the powerline communications line driver circuit shown in [Figure 1](#). Here, the op amp is in a disabled state.

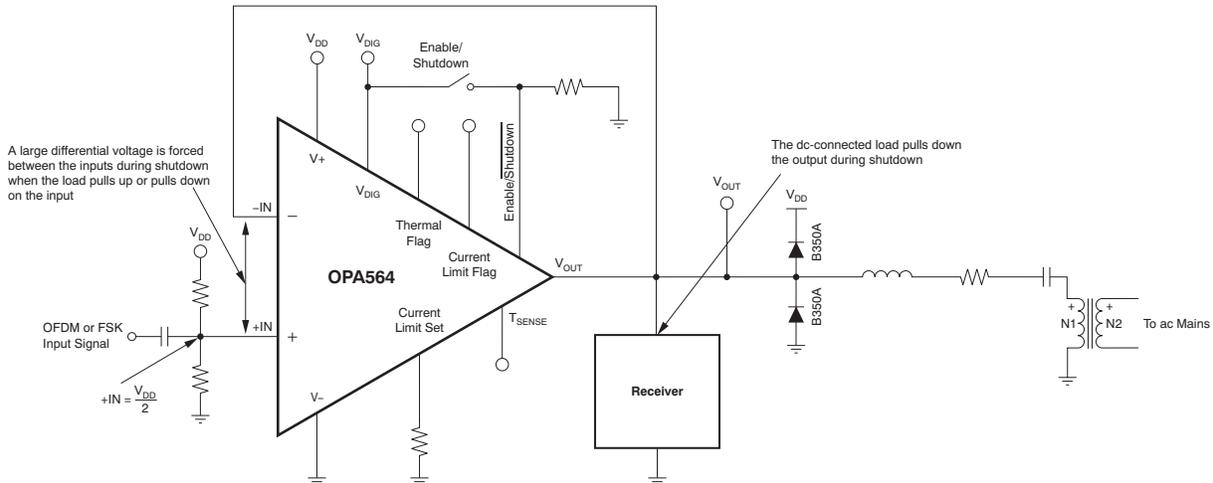

**Figure 1. Unity-Gain Powerline Communications Line Driver with DC-Coupled Load**

This circuit consists of the OPA564 power amplifier (PA) connected in a unity-gain power amplifier configuration. A receiver circuit connects directly to the OPA564 PA output. Connecting the receiver input impedance directly to the amplifier output creates an imbalance between the PA inputs when the PA is placed into the disabled state. [Figure 2](#) compares the PA input and output when a large imbalance is present and when transmitting the signal.

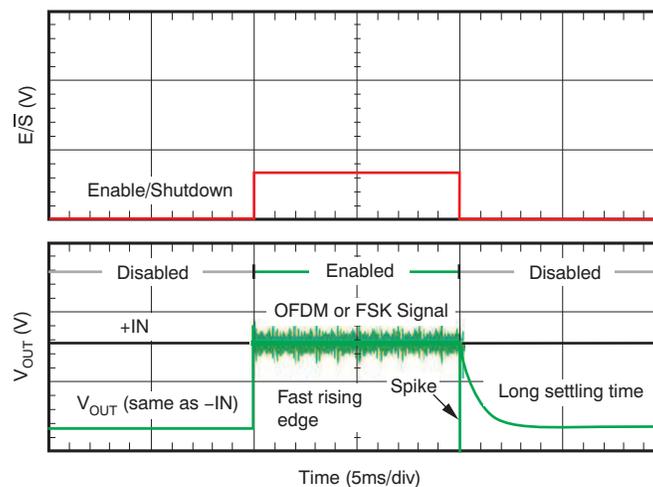

**Figure 2. Output Results for Improperly Configured Circuit**

The first undesirable anomaly shown in [Figure 2](#) is a large voltage difference between the +IN and -IN terminals of the PA. Under extreme conditions, too large of an input differential voltage (greater than 500mV) during the disabled state can cause internal currents to circulate and disrupt the normal bias of the amplifier. This type of behavior may damage the device.

This large difference in voltage between the inputs must be recovered when the PA transitions to the enabled state. The fast rising edge at the beginning of the enabled state can produce higher-order harmonics in the transmitted signal spectrum. After the PA completes the signal transmission and is subsequently disabled, a spike is clearly observed when the inputs terminals are once again being driven apart by several volts. Following the spike, a delay can be seen as the high output impedance of the disabled output stage settles to its final value. Proper circuit configuration during both the enabled and disabled states is necessary to ensure proper and reliable operation of the OPA564.

### 3 Solutions

Fundamentally, the key to any proposed solution is to keep the +IN and -IN potentials as close to each other as practical. Doing so avoids the anomalies shown in Figure 2 and assures long-lasting, reliable device operation.

For the example in Figure 1, one simple solution is to separate the PA output and the receiver input by coupling the receiver with a capacitor. This approach is illustrated in Figure 3 for the unity-gain configuration, and in Figure 4 for an ac-coupled inverting gain configuration.

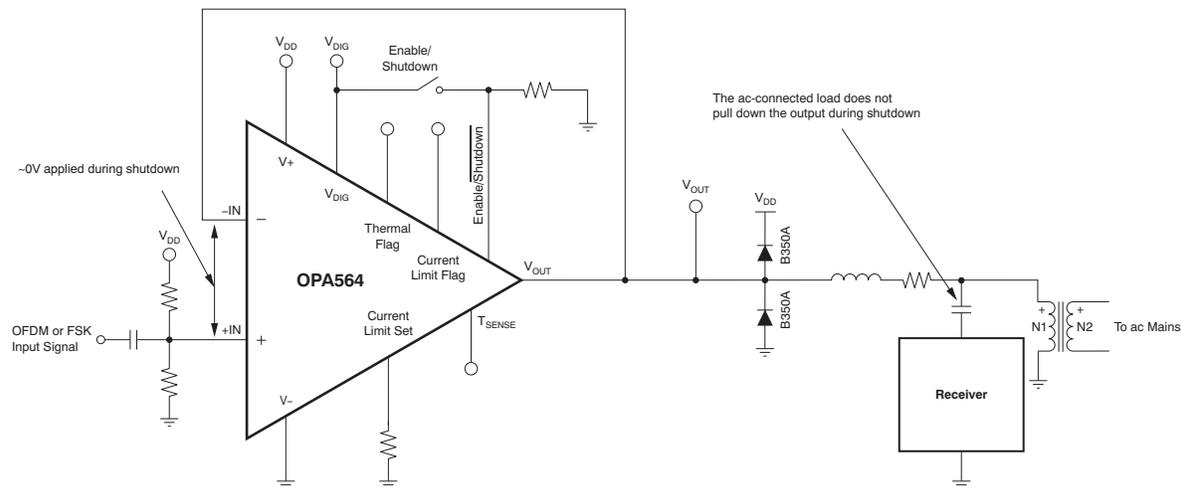


Figure 3. Unity-Gain Powerline Communications Line Driver with AC-Coupled Load

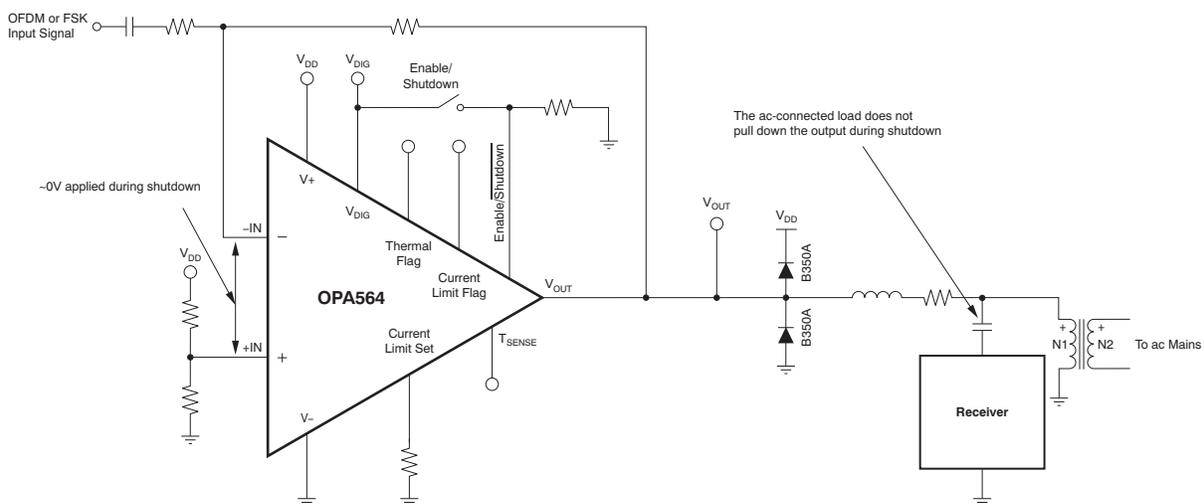


Figure 4. AC-Coupled, Inverting Gain Powerline Communications Line Driver with AC-Coupled Load

Figure 5 shows the results obtained when there are no dc paths that couple the  $-IN$  terminal to ground during the disabled state.

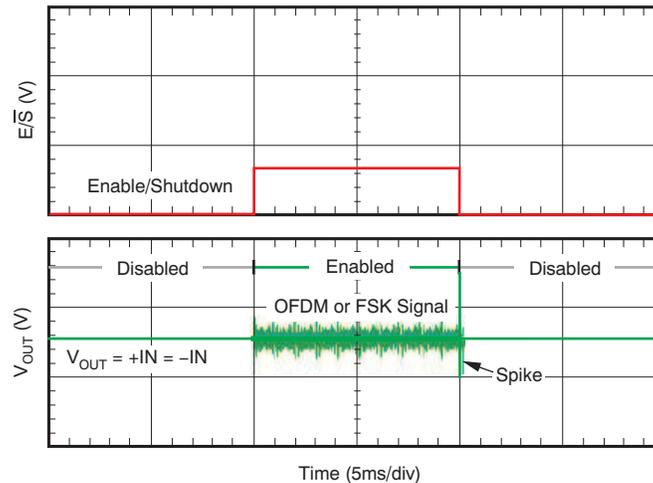


Figure 5. Output Results for Properly Configured Circuit (AC Load Only)

In Figure 5, we can see that the input differential voltage has been eliminated, and the PA transitions from a disabled state to an enabled state, and then returns to a disabled state more quickly. In this example, at the end of the transmission a much smaller spike is still present. This spike is a result of the output stage abruptly switching off and reacting with the complex impedance of the line coupling circuit and electrostatic discharge (ESD) protection diodes. This small spike can be eliminated with the addition of a voltage divider designed to set the  $-IN$  terminal equal to the  $+IN$  terminal during shutdown, as shown in Figure 6. Here, notice that the voltage divider on the PA output must match the ratio of the voltage divider that is used to create the midscale bias point at the  $+IN$  pin in order for the technique to be effective.

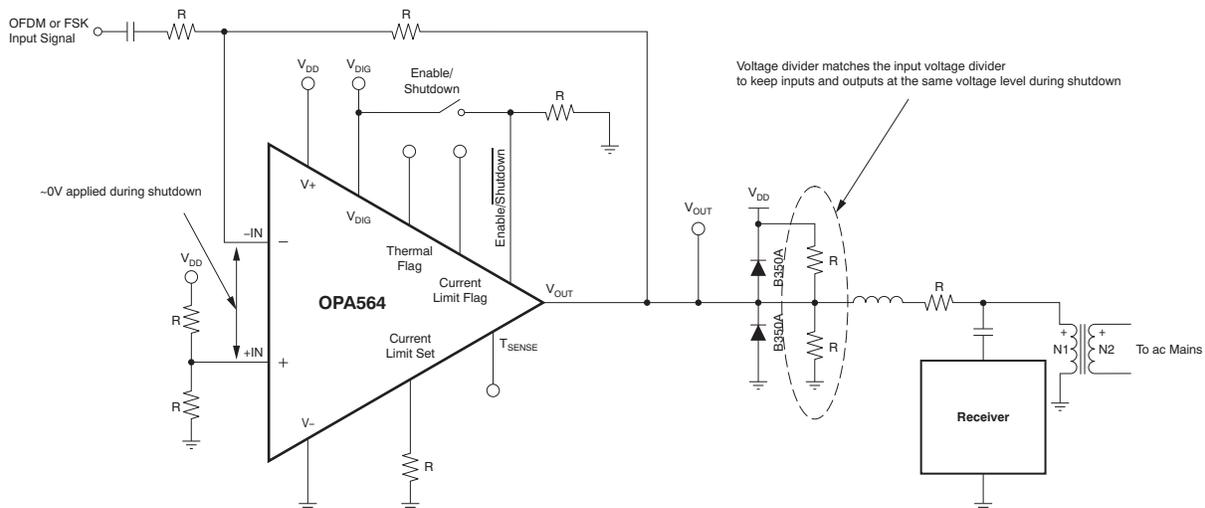


Figure 6. AC-Coupled, Inverting Gain Powerline Communications Line Driver with AC-Coupled Load and Voltage Divider

The presence of the voltage divider has very little effect during transmission because it presents only a very small additional load to the PA output. The resulting output waveforms are shown in Figure 7.

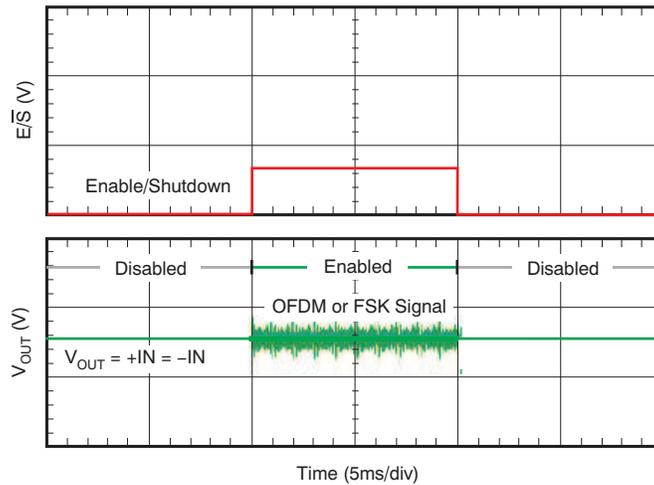


Figure 7. Output Results for Properly Configured Circuit with Voltage Divider

Other applications may require dc biasing of the load in a dual power-supply configuration, as Figure 8 shows.

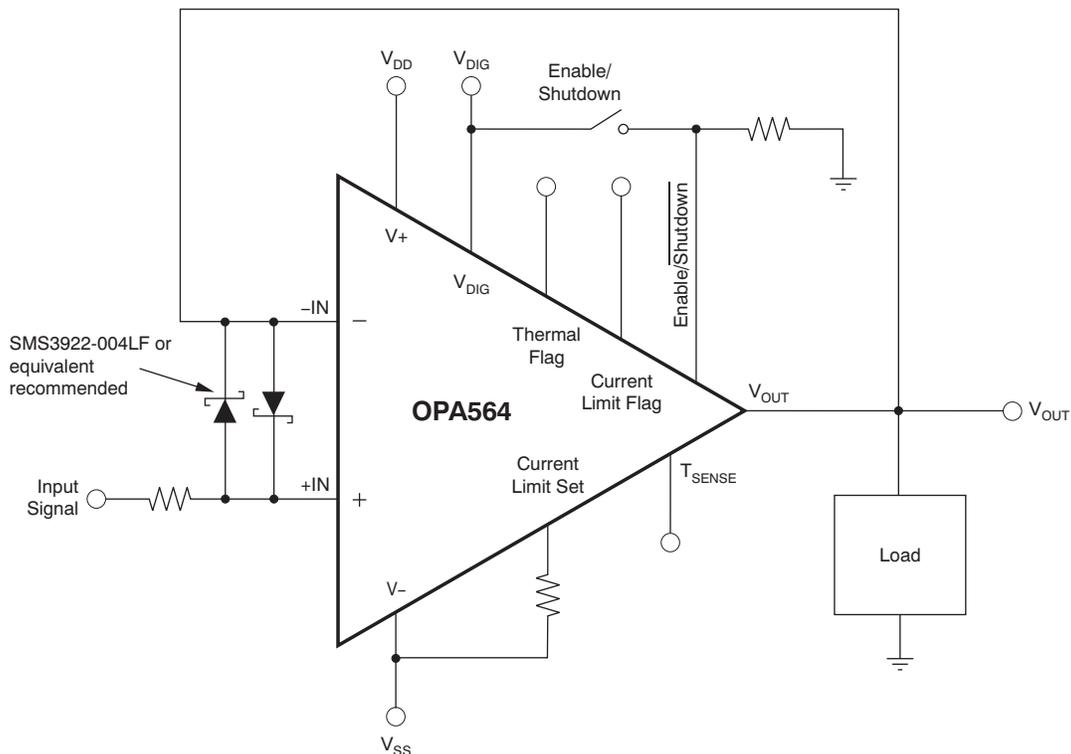


Figure 8. Dual Supply, DC-Connected Load Unity-Gain Follower

In this configuration, it may be necessary to limit the differential input voltage by placing Schottky diodes between the input terminals along with a series-connected, current-limiting resistor.

#### 4 Conclusion

When designing an application with an amplifier that has an enable/shutdown feature such as the OPA564, care must be taken to design the amplifier configuration that allows for proper and reliable operation during both the enabled and disabled states as well as the transitions between these states. While this report presents only a few possible configurations, there are many other configurations that could be equally effective. The key to a proper design is to bias the differential inputs and output as near to the respective voltage levels that each may encounter during normal operation.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated